

- Disable:** To disallow or deactivate a function or circuit.
- Enable:** To allow or activate a function or circuit.
- Fault:** The problem in a nonfunctioning electrical circuit. It is usually due to an open circuit, short circuit, or defective component.
- Float:** A logic level in a digital circuit that is neither HIGH nor LOW. It acts like an open circuit to anything connected to it.
- Gate:** The basic building block of digital electronics. The basic logic gate has one or more inputs and one output and is used to perform one of the following logic functions: AND, OR, NOR, NAND, INVERT, exclusive-OR, or exclusive-NOR.
- Hex:** When dealing with integrated circuits, a term specifying *six* gates on a single IC package.
- Inversion Bar:** A line over variables in a Boolean equation signifying that the digital state of the variables is to be complemented. For example, the output of a two-input NAND gate is written $X = \overline{AB}$.
- Johnson Shift Counter:** A digital circuit that produces several repetitive digital waveforms useful for specialized waveform generation.
- Logic Probe:** An electronic tool used in the troubleshooting procedure to indicate a HIGH, LOW, or float level at a particular point in a circuit.
- Logic Pulsar:** An electronic tool used in the troubleshooting procedure to inject a pulse or pulses into a particular point in a circuit.
- NOT:** When reading a Boolean equation, the word used to signify an inversion bar. For example, the equation $X = \overline{AB}$ is read “X equals NOT AB.”
- Quad:** When dealing with integrated circuits, the term specifying *four* gates on a single IC package.
- Repetitive Waveform:** A waveform that repeats itself after each cycle.
- Troubleshooting:** The work that is done to find the problem in a faulty electrical circuit.
- Truth Table:** A tabular listing that is used to illustrate all the possible combinations of digital input levels to a gate and the output that will result.
- Waveform Generator:** A circuit used to produce specialized digital waveforms.

Problems

Section 3–1

- 3–1. Build the truth table for:
- (a) a three-input AND gate.
 - (b) a four-input AND gate.
- 3–2. If we were to build a truth table for an eight-input AND gate, how many different combinations of inputs would we have?
- 3–3. Describe in words the operation of:
- (a) an AND gate.
 - (b) an OR gate.

Section 3-2

3-4. Determine the logic level at W , X , Y and Z in Figure P3-4.

 


Figure P3-4

3-5. Write the Boolean equation for

- (a) A three-input AND gate
- (b) A four-input AND gate
- (c) A three-input OR gate

3-6. Determine the logic level at W , X , Y and Z in Figure P3-6.

 


Figure P3-6

Section 3-3

3-7. Sketch the output waveform at X for the two-input AND gates shown in Figure P3-7.

 


Figure P3-7

3-8. Sketch the output waveform at X for the two-input OR gates shown in Figure P3-8.

 


Figure P3-8

3-9. Sketch the output waveform at X for the three-input AND gates shown in Figure P3-9.

 


Figure P3-9

C **3-10.** The input waveform at A is given for the two-input AND gates shown in Figure P3-10. Sketch the input waveform at B that will produce the output at X .

 


Figure P3-10

- C** 3–11. Repeat Problem 3–10 for the two-input OR gates shown in Figure P3–11.

 


Figure P3–11

Section 3–4

- 3–12. Using Figure P3–12, sketch the waveform for the *enable signal* that will allow pulses 2, 3 and 6, 7 to get through to the receiving device.

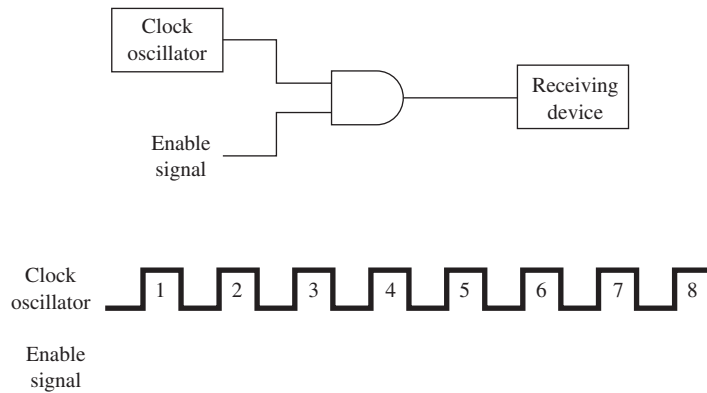


Figure P3–12

- 3–13. Repeat Problem 3–12, but this time sketch the waveform that will allow only the even pulses (2, 4, 6, 8) to get through.

Section 3–5

- 3–14. How many separate OR gates are contained within the 7432 TTL IC?
 3–15. Sketch the actual pin connections to a 7432 quad two-input OR TTL IC to implement the circuit of Figure 3–18.
 3–16. How many inputs are there on each AND gate of a 7421 TTL IC?
 3–17. The 7421 IC is a 14-pin DIP. How many of the pins are *not* used for anything?

Section 3–6

- T*** 3–18. What are the three logic levels that can be indicated by a logic probe?
T 3–19. What is the function of the logic pulser?

*The letter T designates a problem that involves Troubleshooting.

- T** 3–20. When troubleshooting an OR gate such as the 7432, when the pulser is applied to one input, should the other input be connected HIGH or LOW? Why?
- T** 3–21. When troubleshooting an AND gate such as the 7408, when the pulser is connected to one input, should the other input be connected HIGH or LOW? Why?
- C T** 3–22. The clock enable circuit shown in Figure P3–22 is not working. The enable switch is up in the enable position. A logic probe is placed on the following pins and gets the following results. Find the cause of the problem.

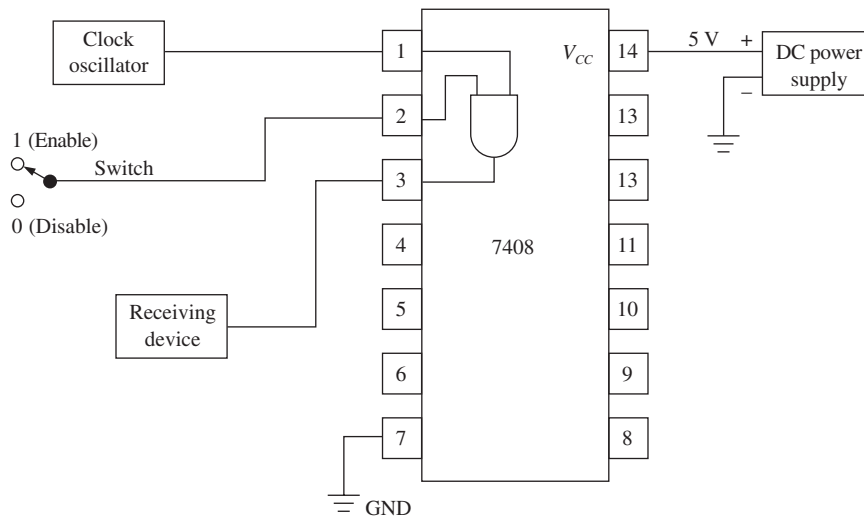


Figure P3–22

Probe on Pin	Indicator Lamp
1	Flashing
2	On
3	Off
7	Off
14	On

- C T** 3–23. Repeat Problem 3–22 for the following troubleshooting results.

Probe on Pin	Indicator Lamp
1	Flashing
2	Off
3	Off
7	Off
14	On

- C T** 3–24. Repeat Problem 3–22 for the following troubleshooting results.

Probe on Pin	Indicator Lamp
1	Flashing
2	On
3	Off
7	Dim
14	On

Section 3-7

3-25. For Figure P3-25, write the Boolean equation at X . If $A = 1$, what is X ?

 


Figure P3-25

3-26. For Figure P3-26, write the Boolean equation at X and Z . If $A = 0$, what is X ? What is Z ?

 


Figure P3-26

3-27. Using Figure P3-26, sketch the output waveform at X and Z if the timing waveform shown in Figure P3-27 is input at A .



Figure P3-27

Section 3-8

3-28. For Figure P3-28, write the Boolean equation at X and Y and build a truth table for each.



Figure P3-28

3-29. Determine the logic levels at W , X , Y and Z in Figure P3-29.

 


Figure P3-29

3-30. Using Figure P3-28, sketch the output waveforms for X and Y , given the input waveforms shown in Figure P3-30. ($X = \overline{AB}$, $Y = \overline{CD}$)

 


Figure P3-30

Section 3-9

3-31. Determine the logic level at W, X, Y and Z in Figure P3-31.

 


Figure P3-31

3-32. Using Figure P3-32, sketch the waveforms at X and Y with the switches in the down (0) position. Repeat with the switches in the up (1) position.

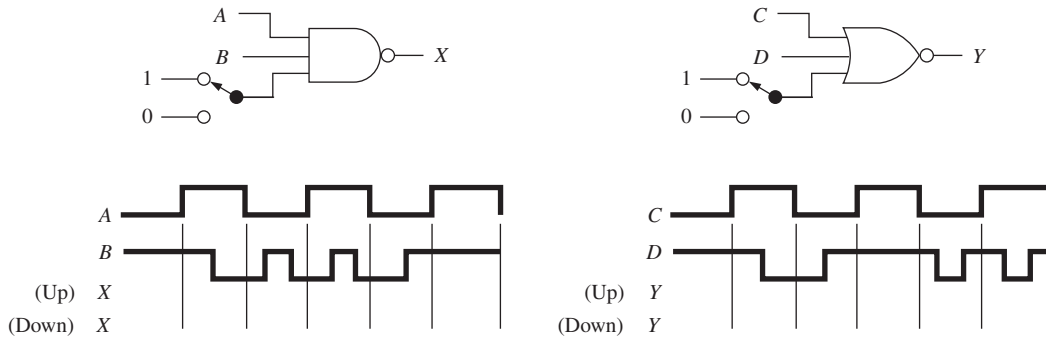


Figure P3-32

3-33. In words, what effect does the switch have on each circuit in Figure P3-32?

3-34. For Figure P3-34, write the Boolean equation at X and Y and build a truth table for each.

 


Figure P3-34